

Inductores y Capacitores

Dpto. de Física, Facultad de Ciencias Físico-Mat. y Nat. (UNSL)

R, L y C sólo dependen de factores geométricos y del material. No Dependen ni de V ni de I ni de q

$$i(t) = (V_0/R)(1 - e^{-t/\tau})$$

$$i(t) = (V_0/R)e^{-t/\tau}$$

$$V_L(t) = V_0 e^{-t/\tau}$$

$$V_L(t) = -V_0 e^{-t/\tau}$$

$$\tau = L/R$$

$$i(t) = (V_0/R)e^{-t/\tau}$$

$$i(t) = -(V_0/R)e^{-t/\tau}$$

$$V_C(t) = V_0(1 - e^{-t/\tau})$$

$$V_C(t) = V_0 e^{-t/\tau}$$

$$\tau = RC$$

Estado Transitorio.



$$I = \frac{V_R}{R}$$

$$V_R = IR$$


$$i_L(t) = \frac{1}{L} \int_{t=0}^{t=t} v_L(t) dt \quad v_L(t) = L \frac{di(t)}{dt}$$

$$i_C(t) = C \frac{dv_C(t)}{dt} \quad v_C(t) = \frac{1}{C} \int_{t=0}^{t=t} i_C(t) dt$$

Válidas para todo tiempo

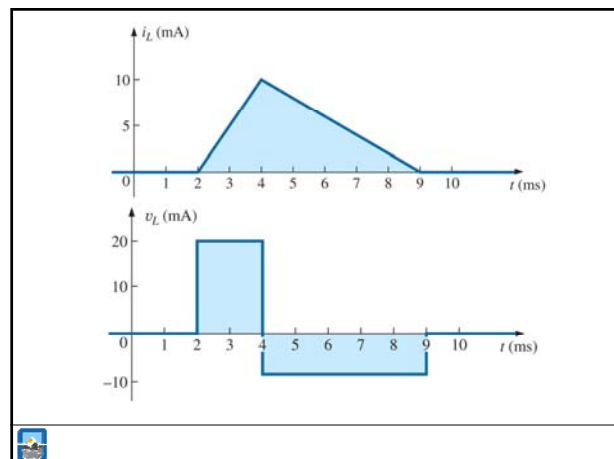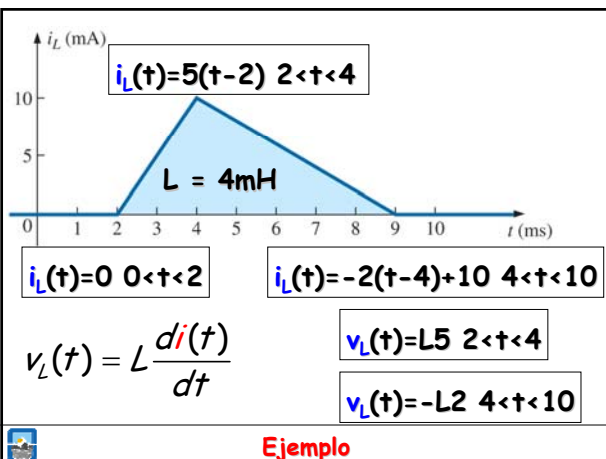



Corriente Alterna (AC)

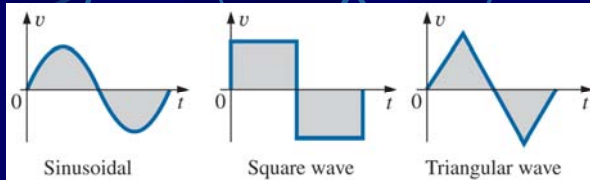

Importancia:



Generador de Corriente Alterna

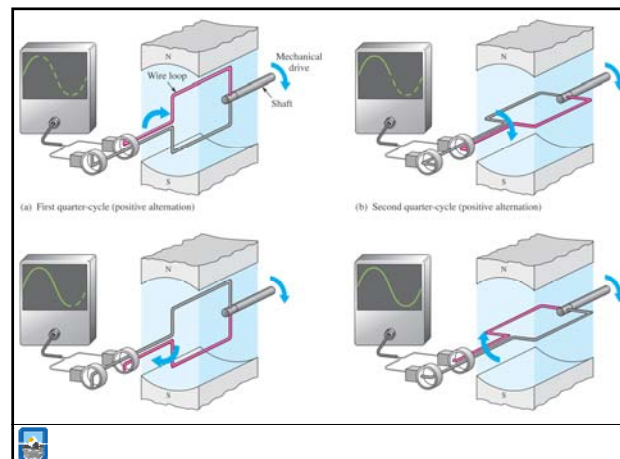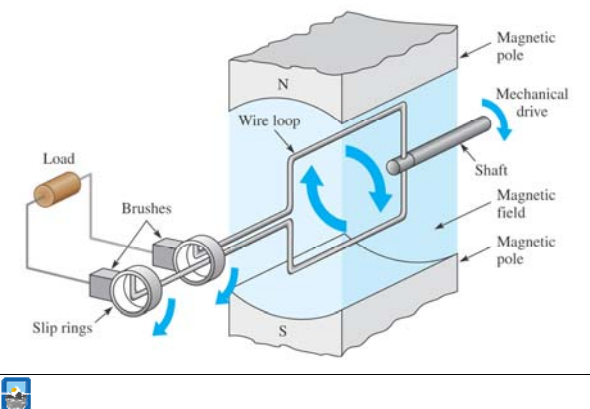


Flujo magnético:

$$\Phi_B = BA \cos \theta$$

Ley de Faraday:
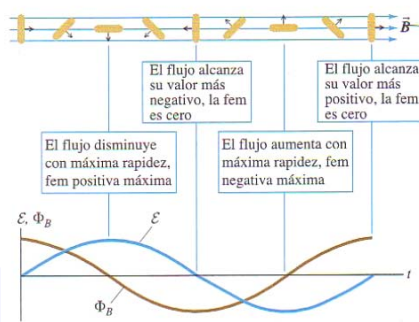
$$\epsilon = -N \frac{\Delta \Phi_B}{\Delta t}$$



Flujo magnético:

$$\Phi_B = BA \cos \theta$$

$$\theta = \omega t$$







Ley de Faraday:







$$\epsilon = -N \frac{\Delta \Phi_B}{\Delta t}$$



$$\epsilon(t) = (NAB\omega) \sin(\omega t)$$

$$\epsilon_{Máx} = NAB\omega$$
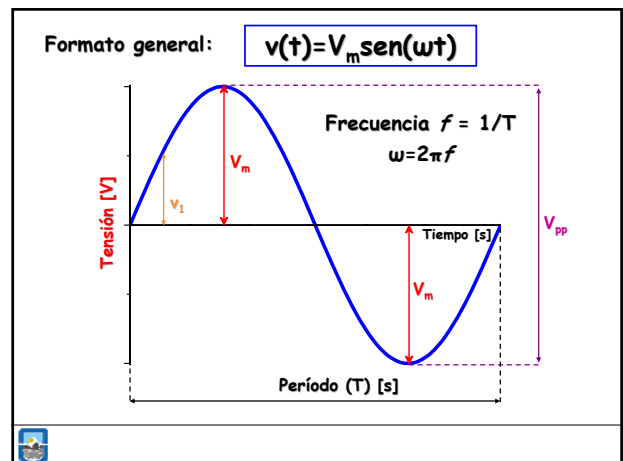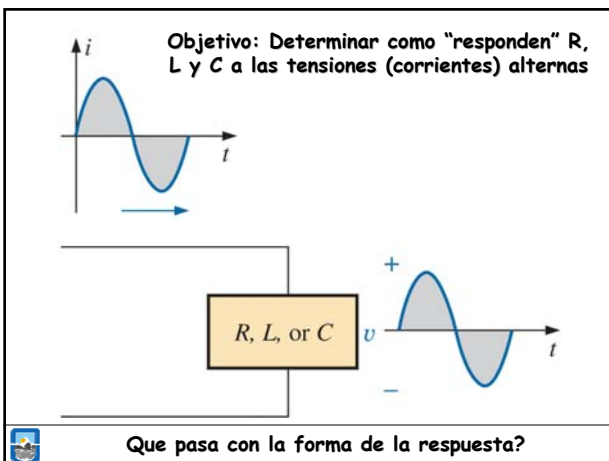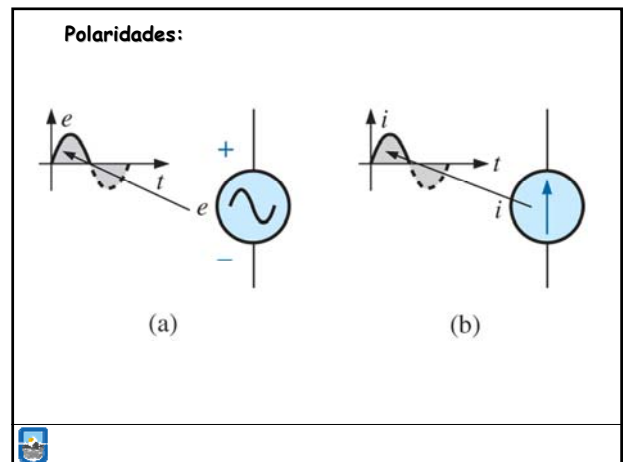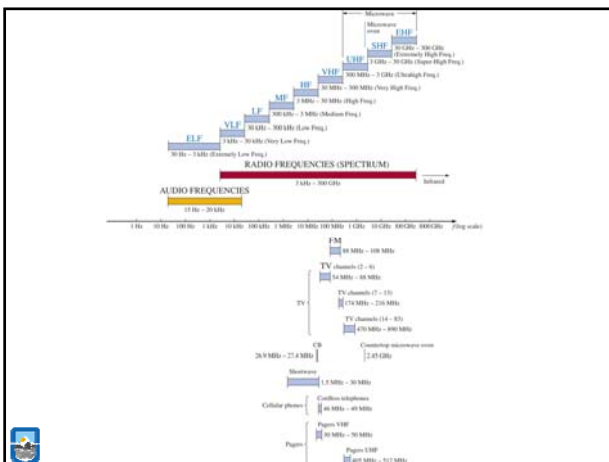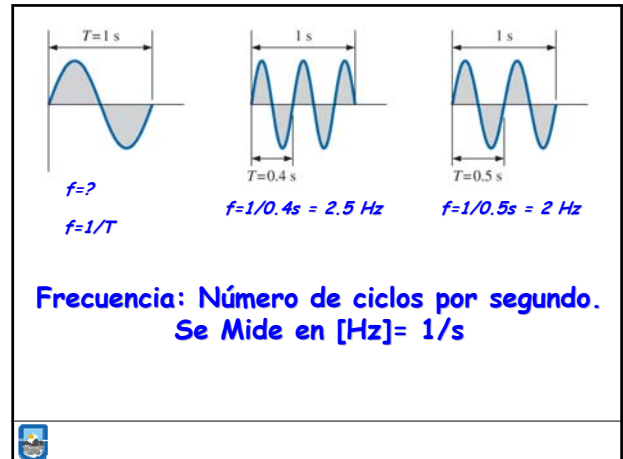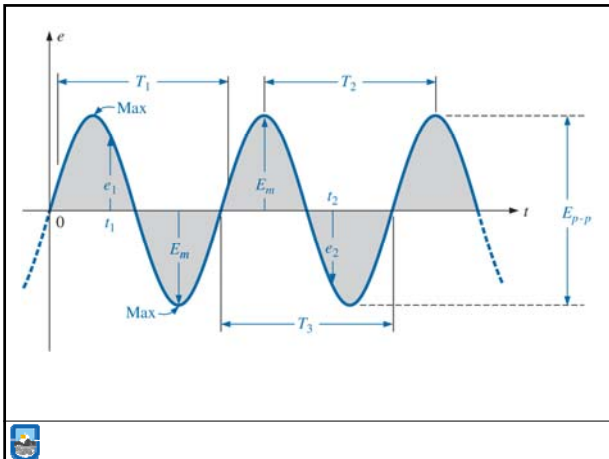
$$\epsilon(t) = \epsilon_{Máx} \sin(\omega t)$$






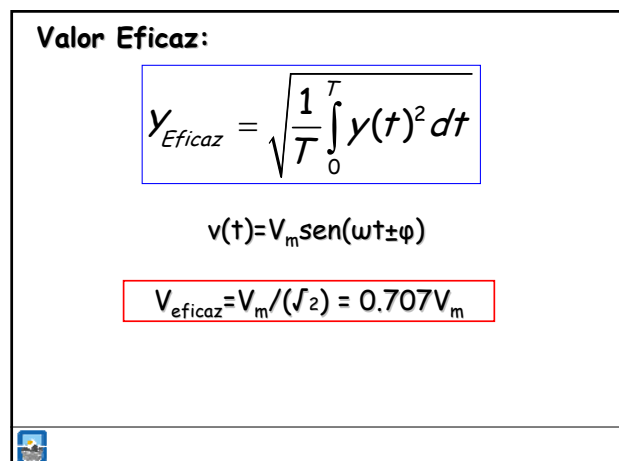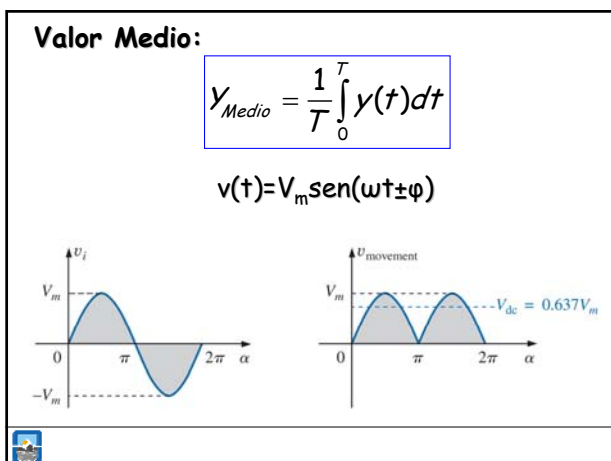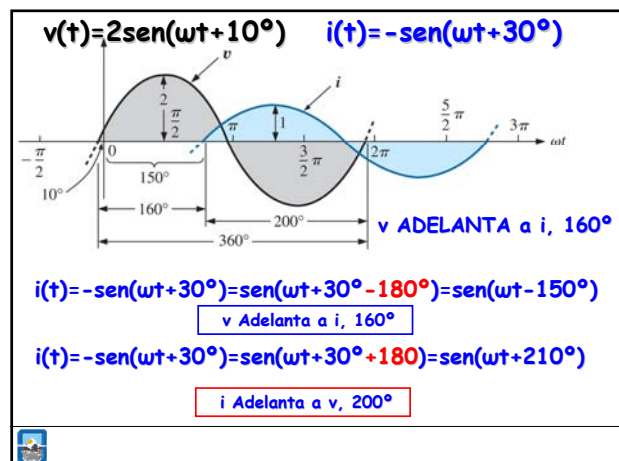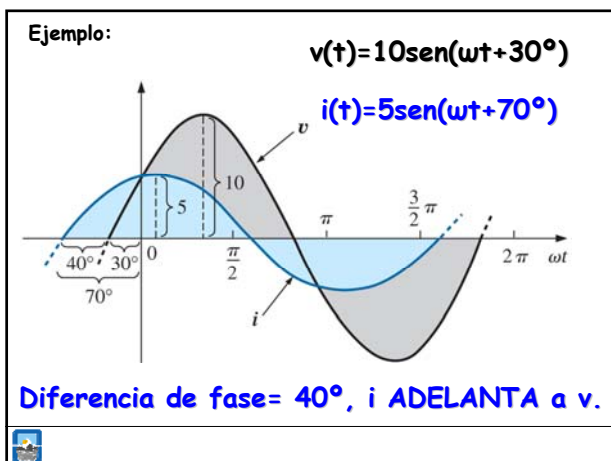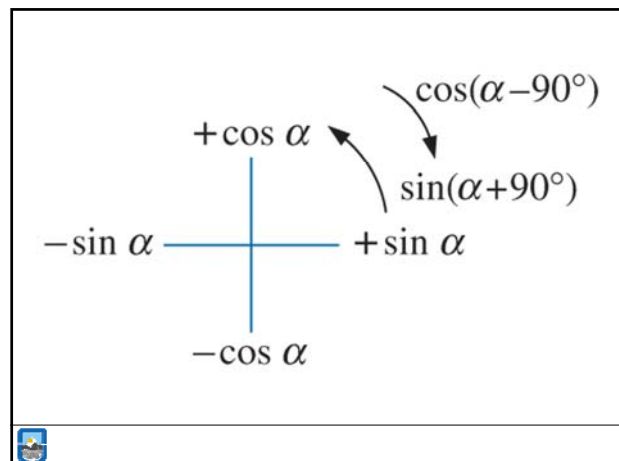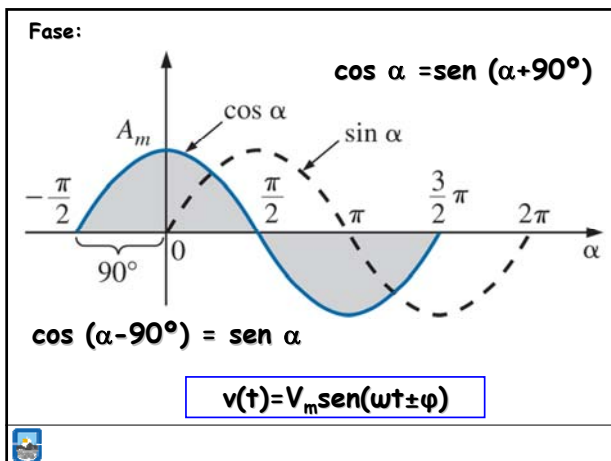

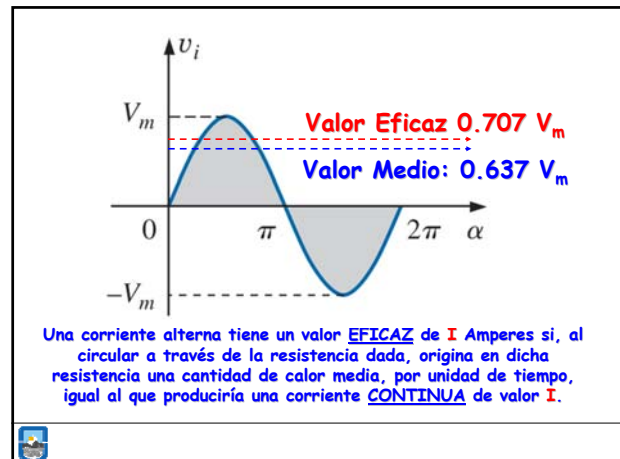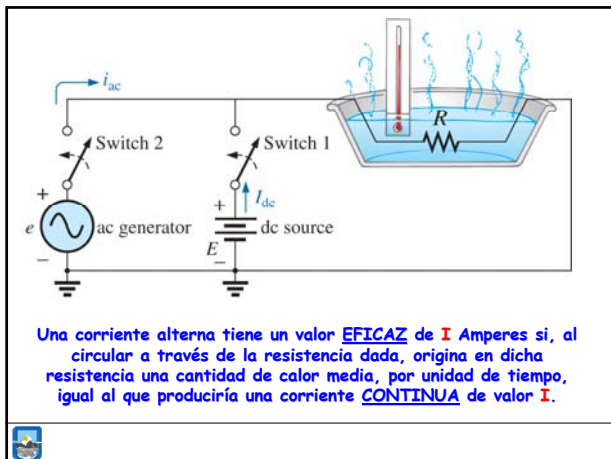

Respuesta de R, L y C a la Corriente Alterna. Fasores.

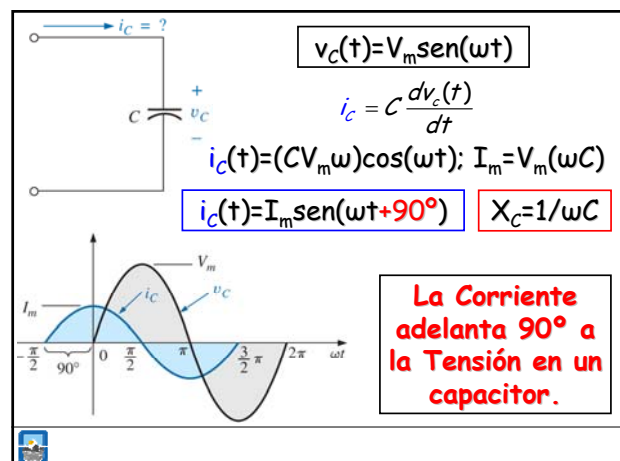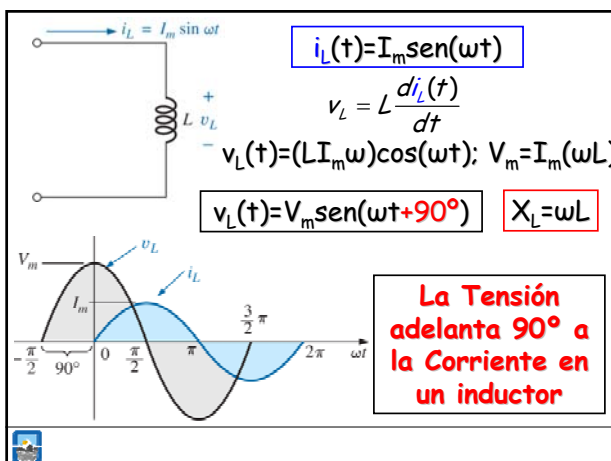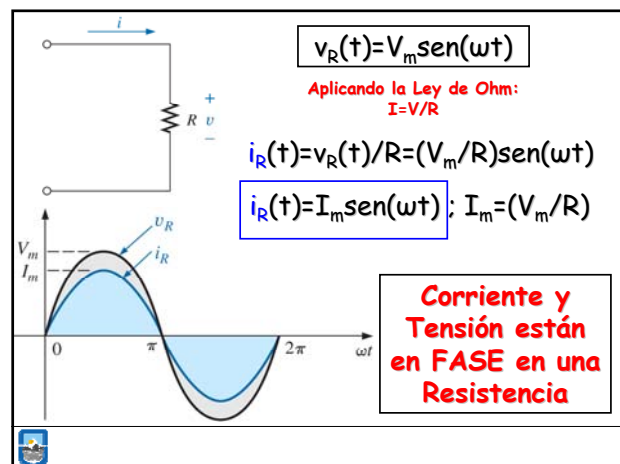Dpto. de Física, Facultad de Ciencias Físico-Mat. y Nat. (UNSL)



Ejemplo: Dada la corriente a través de un inductor de 0.1 H. Determine $v_L(t)$.

$$i_L(t) = I_m \sin(\omega t)$$

$$v_L(t) = V_m \sin(\omega t + 90^\circ)$$

$$i_L(t) = 10 \sin(377t)$$

$$V_m = I_m X_L$$


$$X_L = \omega L$$

$$I_m = 10 \text{ A} ; \omega = 377 \text{ rad/s}$$

$$X_L = (377 \text{ rad/s})(0.1 \text{ H}) = 37.7 \, \Omega$$

$$V_m = (10 \text{ A})(37.7 \, \Omega) = 377 \text{ V}$$

$$v_L(t) = 377 \sin(377t + 90^\circ)$$

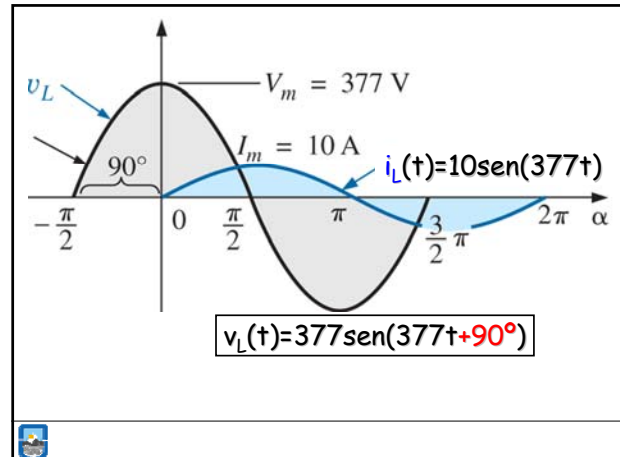

Notación Fasorial:

$$y(t) = Y_m \sin(\omega t + \phi)$$


$$\Rightarrow \mathbf{Y} = Y_{\text{Eficaz}} \angle \phi^\circ$$

$$v_R(t) = V_m \sin(\omega t)$$

$$\Rightarrow \mathbf{V}_R = V_R \angle 0^\circ$$

$$i_R(t) = I_m \sin(\omega t)$$
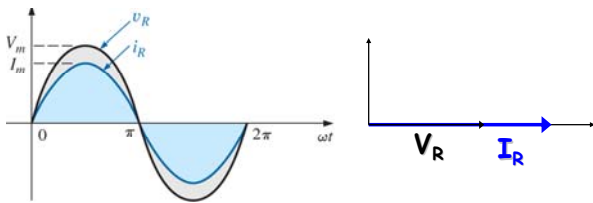
$$\Rightarrow \mathbf{I}_R = I_R \angle 0^\circ$$



$$\mathbf{V}_R = V_R \angle 0^\circ$$

Ley de Ohm: $\mathbf{I} = \frac{\mathbf{V} \angle 0^\circ}{R \angle \phi_R}$

$$\phi_R = 0^\circ \Rightarrow \mathbf{I} = \frac{V \angle 0^\circ}{R \angle 0^\circ} = \frac{V}{R} \angle (0^\circ - 0^\circ) = \frac{V}{R} \angle 0^\circ$$

$$\mathbf{Z}_R = R \angle 0^\circ$$

Impedancia Resistiva


Circuito Inductivo:

$$v_L(t) = V_m \sin(\omega t) \rightarrow \mathbf{V}_L = V \angle 0^\circ$$

Ley de Ohm: $\mathbf{I}_L = \frac{\mathbf{V}_L \angle 0^\circ}{X_L \angle \phi_L} = \frac{V_L}{X_L} \angle (0^\circ - \phi_L)$ $\phi_L = 90^\circ$

$$\mathbf{I}_L = \frac{V_L}{X_L} \angle (0^\circ - 90^\circ) = \frac{V_L}{X_L} \angle -90^\circ \quad \mathbf{I}_L = I \angle -90^\circ$$

$$\mathbf{Z}_L = X_L \angle 90^\circ$$

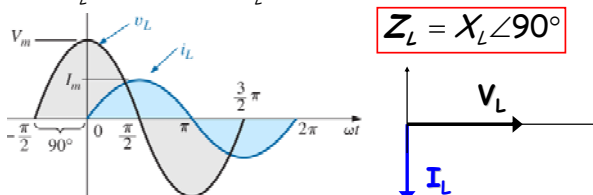

Circuito Inductivo:


$$\mathbf{V}_L = V \angle 0^\circ$$

$$\mathbf{I}_L = I \angle -90^\circ$$

$$\mathbf{V}_L = V \angle 90^\circ$$

$$\mathbf{I}_L = I \angle 0^\circ$$

$$\mathbf{Z}_L = X_L \angle 90^\circ$$

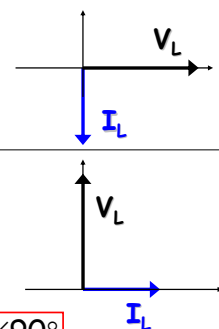

Circuito Capacitivo:
 $v_c(t) = V_c \sin(\omega t) \rightarrow V_c = V \angle 0^\circ$

Ley de Ohm: $I_c = \frac{V_c \angle 0^\circ}{X_c \angle \phi_c} = \frac{V_c}{X_c} \angle (0^\circ - \phi_c)$ $\phi_c = -90^\circ$

$I_c = \frac{V_c}{X_c} \angle (0^\circ - (-90^\circ)) = \frac{V_c}{X_c} \angle 90^\circ$ $I_c = I \angle 90^\circ$

$Z_c = X_c \angle -90^\circ$

Ejemplo: Utilizando álgebra compleja determine la corriente del circuito. Grafique.

$v = 24 \sin(\omega t) \Rightarrow V = \frac{24}{\sqrt{2}} \angle 0^\circ = 16.968 \angle 0^\circ$

$X_L = 3 \Omega$

$I = \frac{V}{Z_L} = \frac{V \angle 0^\circ}{X_L \angle 90^\circ} = \frac{16.968 \angle 0^\circ}{3 \Omega \angle 90^\circ} = 5.656 \angle -90^\circ$

$i(t) = \sqrt{2}(5.656) \sin(\omega t - 90^\circ) = 8 \sin(\omega t - 90^\circ)$

Impedancias en Serie:

$Z_T = Z_1 + Z_2 + Z_3 + \dots + Z_N$

Ejemplo: Determine la Z_T :

$R = 4 \Omega$ $X_L = 8 \Omega$

$Z_T = Z_1 + Z_2$
 $= R \angle 0^\circ + X_L \angle 90^\circ$
 $= R + jX_L = 4 \Omega + j8 \Omega$
 $Z_T = 8.944 \Omega \angle 63.43^\circ$

Triángulo de Impedancias

$Z_T = Z_1 + Z_2 + Z_3$
 $= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ$
 $= R + jX_L - jX_C$
 $= R + j(X_L - X_C) = 6 \Omega + j(10 \Omega - 12 \Omega) = 6 \Omega - j2 \Omega$
 $Z_T = 6.325 \Omega \angle -18.43^\circ$

Ley de Ohm en AC:

$$I = \frac{V}{Z}$$

OJO!!! V e I son FASORES!!!

