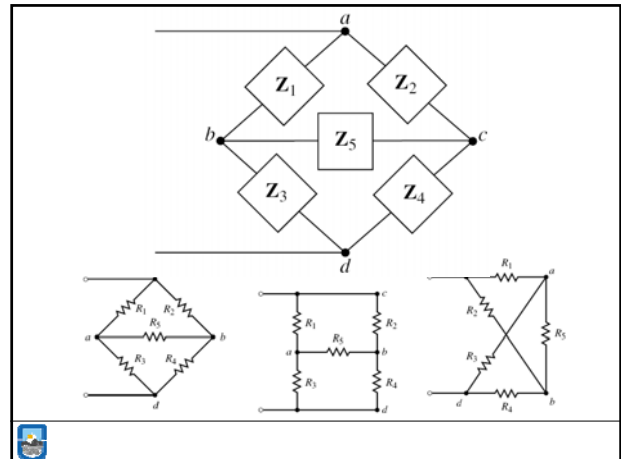


Circuitos Puentes.



Dpto. de Física, Facultad de Ciencias Físico-Mat. y Nat. (UNSL)



Cuando la I por Z_5 es nula el puente está balanceado. Entonces:

$$V_{ab} = (Z_5)(0A) = 0V$$

$$I_{Z_1} = I_{Z_3} = \frac{V_{cd}}{Z_1 + Z_3} \quad I_{Z_2} = I_{Z_4} = \frac{V_{cd}}{Z_2 + Z_4}$$

$$V_{ad} = V_{bd} \rightarrow Z_3 I_{Z_3} = Z_4 I_{Z_4} \quad Z_3 \left(\frac{V_{cd}}{Z_1 + Z_3} \right) = Z_4 \left(\frac{V_{cd}}{Z_2 + Z_4} \right)$$

$$\frac{Z_3}{Z_1 + Z_3} = \frac{Z_4}{Z_2 + Z_4} \quad \frac{Z_1}{Z_3} + 1 = \frac{Z_2}{Z_4} + 1$$

$$\boxed{\frac{Z_1}{Z_3} = \frac{Z_2}{Z_4}}$$

$$Z_x = \frac{Z_2 Z_3}{Z_1}$$

$$= \frac{(10 \text{ k}\Omega)(100 \Omega)}{30 \text{ k}\Omega \angle -20^\circ}$$


$$= 33.3 \Omega \angle 20^\circ$$

$$= 31.3 + j11.4 \Omega$$


Determine R_x y L_x :

$$R_x = 31.3 \Omega$$
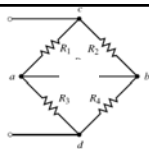
$$L_x = \frac{X_L}{2\pi f} = \frac{11.4 \Omega}{2\pi(1000 \text{ Hz})} = 1.81 \text{ mH}$$



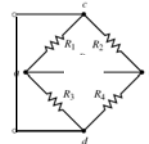
$$R_{\text{Equivalente}} = (R_1 + R_2) // (R_3 + R_4)$$



$$R_{\text{Equivalente}} = R_1 // R_3 + R_2 // R_4$$

Puente de Maxwell:

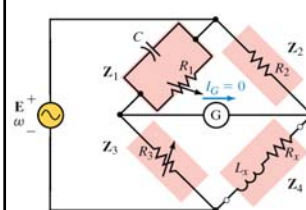

Sirve para determinar la inductancia y la resistencia serie de un inductor.

$$X_L < R$$

R_1 y R_3 son ajustadas hasta que $I_G = 0$


$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$

$$\left[\frac{(R_1) \left(-j \frac{1}{\omega C} \right)}{R_1 - j \frac{1}{\omega C}} \right] = \frac{R_3}{R_x + j\omega L_x}$$

$$L_x = R_2 R_3 C$$

$$R_x = \frac{R_2 R_3}{R_1}$$

Puente de Hay:

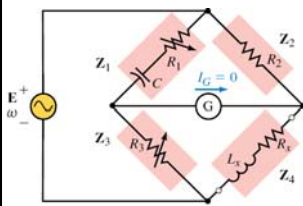


$$X_L > R$$

$$L_x = \frac{R_2 R_3 C}{\omega^2 R_1^2 C^2 + 1}$$

$$R_x = \frac{\omega^2 R_1 R_2 R_3 C^2}{\omega^2 R_1^2 C^2 + 1}$$



Puente de Schering:

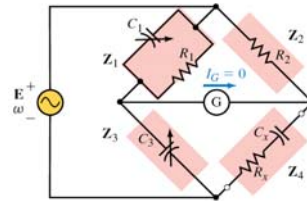

Sirve para
determinar el
valor de un
capacitor
desconocido.

$$C_x = \frac{R_1 C_3}{R_2}$$

$$R_x = \frac{C_1 R_2}{C_3}$$

